

Logic Design (Part 2)

Combinational Logic Circuits (Chapter 3 + Notes)

Based on slides © McGraw-Hill
Additional material © 2004/2005/2006 Lewis/Martin
Additional material © 2008 Roth
Additional material © 2010 Taylor
Additional material © 2013 Farmer
Additional material © 2018 Narahari

1

Next

- Download Set1 of Cedar Logic or LogiSim examples
 - From lectures webpage
- Designing combinational logic circuits
 - Cedar Logic or LogiSim
- Intro to Combinational logic devices
 - Building complex devices using the basic gates
 - Adders, Multiplexers, Decoders,.....

2

Digital Logic Design – Introduction

- MOS transistors used as switches to implement basic logic gates (boolean operations)
 - (NAND, NOT, AND, OR,...).
- Boolean logic functions operate on boolean variables
 - expressed with AND, OR, and NOT
 - (A AND B) OR (NOT A AND C)
 - AND, OR, NOT notation replaced by . + ' ◦ $(A.B) + (A' . C)$
- Boolean function represented as:
 - Truth table
 - logic circuit

3

Digital Logic Circuits

- We saw how we can build the simple logic gates using transistors
- Can build **any** boolean function using these gates
- Use these gates as building blocks to build more complex combinational circuits
 - Multiplier, Multiplexer, Decoder,
 - ...any boolean function
- Develop a theoretically sound approach to designing boolean functions and circuits....**Boolean Algebra**

4

Definition: Combinational and Sequential Logic Circuits

- A circuit is a collection of devices that are physically connected by wires
 - Combinational circuit
 - Sequential circuit
- In Combinational circuit the input determines output
- In sequential circuit, the input and the previous 'state' (previous values) determine output and next 'state'
 - Need to 'remember' previous value – need **memory** device
 - Need circuit to implement concept of storage
- Start with design of Combinational Logic circuits

5


Boolean Function..Recall from Discrete Math!

- Output(s) is a function on input boolean variables
- $z = f(x, y, \dots)$
- x, y are *boolean variables* (0 or 1)
- $z=f(x, y)$ is a *boolean output*
- The “operators” used are any of the boolean logic operators
 - AND, OR, NOT, NAND, etc.
- **If integers are represented using binary notation, then all functions over integers are boolean functions**
- How do we represent boolean functions?

6

Boolean Functions

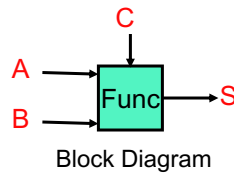- A function can be thought of as a mapping from inputs to outputs.
 - Think of a black box with n binary inputs and 1 binary output
- We can express the action of this function in terms of a **truth table** which says what the output should be for every input pattern.
- This function implements a binary adder!



Truth table
(describes behavior)

A	B	C	S
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

7

Boolean Algebra

- George *Boole* – Famous Mathematician/Logician
 - **Boolean Algebra** – branch of Algebra, where variables can only have values of true (1) or false (0)
 - Boolean operators: AND(.), OR(+), NOT(~ or !)
- With Boolean Algebra:
 - We create “functions” using boolean variables and operators
 - Any logical function can be expressed in terms of the three elementary operations: AND, OR and NOT
 - Boolean functions can be **rearranged** and sometimes **simplified** by applying algebraic identities
 - DeMorgan’s laws: allow conversion from AND to OR (using NOT)
- Big idea – you can write a logical function as a boolean algebraic expression and then use various identities to rewrite that function in an equivalent (usually simpler) form.

8

DeMorgan's Law: Converting AND to OR with help from NOT


- $\text{NOT}(A \text{ AND } B) = (\text{NOT } A) \text{ OR } (\text{NOT } B);$
- $\text{NOT}(A \text{ OR } B) = (\text{NOT } A) \text{ AND } (\text{NOT } B);$
- In C syntax: $\sim(A\&B) = \sim A|\sim B$ $\sim(A|B) = \sim A\&\sim B$

A	B	$\sim A$	$\sim B$	$\sim A\&\sim B$	$(A\&B)$	$\sim A \sim B$	$(A B)$	$\sim(A B)$	$\sim(A\&B)$
0	0	1	1	1	0	1	0	1	1
0	1	1	0	0	0	1	1	0	1
1	0	0	1	0	0	1	1	0	1
1	1	0	0	0	1	0	1	0	0

9

DeMorgan's Law

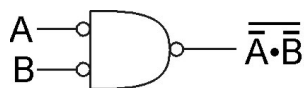- Converting AND to OR (with some help from NOT)
- Consider the following gate:



From DeMorgan's laws:
 $\text{NOT}((\text{NOT } A) \text{ AND } (\text{NOT } B)) =$
 $\text{NOT}(\text{NOT } A) \text{ OR } \text{NOT}(\text{NOT } B) =$
 $A \text{ OR } B$

A	B	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$\overline{\overline{A} \cdot \overline{B}}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

Same as $A+B$

*To convert AND to OR
(or vice versa),
invert inputs and output.*

10


Representation of Boolean Logic Functions

✧ A logic function can be represented as

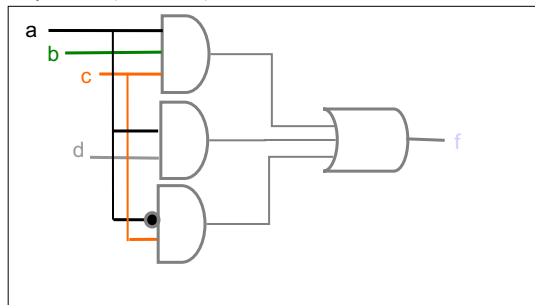1. a truth table or
2. a logic expression or
3. a logic circuit

✧ Example

$$f = a.(b.c + d) + \bar{a}.c = a.b.c + a.d + \bar{a}.c$$



a	b	c	d	f
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

11

Completeness: Very Important Concept

- It can be shown that any truth table (i.e. any binary function of binary variables) can be reduced to combinations of the AND & NOT functions, or of the OR & NOT functions.
 - This result extends also to functions of more than two variables
- In fact, it turns out to be convenient to use a basic set of three logic gates:
 - AND, OR & NOT or NAND, NOR & NOT
 - In fact, can implement all logic functions using just NAND!
- Question to ask: How do we design a good circuit ?

12

Truth Tables to Boolean Function/Circuits

- A truth table can be mapped to a Boolean function
 - In **Disjunctive Normal Form (DNF)** – an OR of AND terms
 - Recall from Discrete 1 (CS1311)
- Each row in the truth table corresponds to a conjunction of literals (i.e., Boolean variables) and is called *minterm*
 - Literal is Boolean variable A or its complement A'
- To derive the Boolean function F:
 - Examine each row where the output = 1
 - Include this conjunctive term as an AND of the literals
 - F = OR of the included terms (minterms)
 - Also called sum of products (OR of minterms)

13

Truth Tables to Boolean Function

- Input variables: A,B,C (Notation: NOT A written as A')
- Output = F
- First examine rows where F=1
- F=1 when A=0 B=1 C=0
 - bool func is (A' AND B AND C')
- F=1 when A=1 B=0 C=0
 - bool func is (A AND B' AND C')
- F=1 when A=1 B=1 C=0
 - bool func is (A AND B AND C')
- F=0 on all other input combinations
- Write F as OR of above minterms
- F = (A'.B.C') OR (A.B'.C') OR (A.B.C')

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

14

Boolean functions, Circuits & Boolean Algebra!

▪ Power of abstraction....To build boolean functions, you can work with basic gates..no need to go down to the transistor level !!

▪ what is the theory behind boolean logic design ?

- Boolean Algebra

- DeMorgan's Law: Convert AND&NOT to OR&NOT
 - $(\text{NOT } A) \text{ AND } (\text{NOT } B) = \text{NOT } (A \text{ OR } B)$ (i.e., A NOR B)
 - $(\text{NOT } A) \text{ OR } (\text{NOT } B) = \text{NOT } (A \text{ AND } B)$ (i.e., A NAND B)
- Disjunctive Normal Form (DNF), etc.

- Question: How can we design an “efficient” circuit to implement a Boolean function ?

- “efficient” = minimum number of logic gates

- Example:

- Given $F = A'BC' + A'B'C + ABC' + AB'C$: 4 AND gates & OR gate
- From Bool Alg., this is equivalent to $F = BC' + B'C$: 2 AND gates & 1 OR gate

15

Boolean Algebra and Combinational Logic Design

- Boolean Logic is a Boolean Algebra

- laws of Boolean Algebra can be applied

- How do we design “efficient” circuits ? Is there a methodology we can follow ?

- Boolean algebra (Karnaugh Maps)
- Again, recall from CS1311 Discrete 1 !

- Reading Assignment: Review Boolean algebra and

- Karnaugh Maps concepts and application to digital logic design

- Notes posted on website

16

How to design combinational circuit

- Analyze the problem
 - Determine inputs and outputs (they must be binary)
- Determine boolean variables
 - inputs x_1, x_2, \dots
 - Outputs y_1, y_2, \dots
- Derive truth table
 - Value of each y_i for each combination of inputs x_1, x_2, \dots
- For simple circuit, find DNF from truth table
- To find 'optimal' (minimum size) 2-level circuit, derive Karnaugh map and find terms

17

Time to test your circuit design&analysis skills...

Analyze Circuits to derive Boolean functions

Design circuits from truth table/function

- In Cedar Logic: Download and open Set1.cdl in CedarLogic
 - Has number of 'pages' of circuits
- In Logisim: Download Set1.zip into folder, it has several Logisim circuits
 - Labelled Set1-Page1.circ, Set1-Page2, etc.
 - Open in Logisim
- Work through the 6 pages of circuits

18

Transistor Circuits...Circuits on Page 1,2,3,4....

- Open in Cedar Logic – view Page 1 circuit
- *UsefulTip (for CedarLogic): Hit space key to center and maximize the circuit in the cedar logic window*
- Circuit on Page 1 is NAND gate (from transistors)
 - Inputs: A,B . can be set to 1 (red) or 0 (black) by clicking on them
 - Output C=1 if at least one of upper two (switches) close
 - This happens when A=0 or B=0 since it is a P-type transistor
 - Output C=0 when A=1 and B=1 since there is a path from C to ground (0) and N type transistor
- Transistors at bottom of page
 - N-type: if input is 1 (red) then transistor close (i.e., short circuit)
 - P-type: if input is 0 (black) then transistor closed (i.e, short circuit)

19

Questions...Circuit on Set1-Page2, Page3, Page4

- Page 2: What gate/function is being implemented?
 - Can you determine this by analyzing the circuit (*instead of deriving truth table*)
 - Note serial structure in upper two transistors = both must close for a path from Power to output, i.e., for output to be = 1
 - Note parallel structure in lower two transistors = at least one must be closed for a path from Ground (0) to output, i.e., for output =0
- Page 3: combination of Page 2 circuit whose output goes to another circuit
- Page 4: What function ? Derive truth table with inputs A,B and 'outputs' C,D, F
 - Is this a standard function ?

20

Circuits with logic gates...Set1 - Pages 5,6,7,8

- Page 5: example using logic gates
- Input specified using the switches
- Output goes to LED (red=1, black=0)
- To determine the function being implemented by a circuit you can “trace” back from output to inputs

21

Questions: Pages 6, 7, 8:

- Page 6: what Boolean functions are being implemented by circuits (a) and (b) ?
- Page 7: Draw circuit to implement the function:
 - $F = (A \text{ AND } (B \text{ XOR } C)) \text{ OR } (\text{NOT } C)$
 - Draw by hand first, then implement in simulator
- Page 8: Design circuit for truth table shown here
 - Derive function and draw by hand first
 - Implement in simulator

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

22

Logic control for overhead light

- Design logic for light switch in a room based on the position of two switches – switches are at two different entrances to the room and either switch should be able to change the state (on/off) of the light independently.
 - If both switches are in the “down” position (represented by 0) the light must be off (represented by 0)
 - No matter what position the switches are in or the current state of the light, flipping either switch must change the state of the light.
- Design gate level circuit
- Complete truth table first

23

Recall our Goal....

- Design a machine that translates from natural language to electrons running around to solve the problem
 - We now have a device that controls how electrons run around
- Next: we want to build a computer
 - First step: Design a collection of logic devices that implement important functions that will be needed to build our computer
- S/W Analogy: When you write your software, you are using a collection of concepts, tools, IDEs and libraries
 - Each has been built, and tested, for you
 - All you have to do is combine them!

24

Next: Combinational Logic Devices

- We saw how we can build the simple logic gates using transistors
- Can build **any** boolean function using these gates
- Use these gates as building blocks to build more complex combinational circuits
 - Decoder: based on value of n-bit input control signal, select one of 2^N outputs
 - Multiplexer: based on value of N-bit input control signal, select one of 2^N inputs.
 - Adder: add two binary numbers
 - ...any boolean function
- **SW Analogy: We are building a library of functions**
 - To design your solution, you can use any device in the library!